

**Department of Computer Science**  
**Forman Christian College**  
**(A Chartered University)**  
**Lahore**



**Digital Logic Design**  
**COMP 206**

# DIGITAL LOGIC DESIGN

## COMP 206

### LAB 6- RUBRIX

DESCRIPTION	MARKS ALLOCATED
Attendance	5%
Proper handling of components, ICs and wiring	20%
Hardware wired completely( for all circuits)	30%
Data table 1	10%
Data Table 2	10%
Data Table 3	5%
Data Table 4	10%
End questions	10%

**Marks will be deducted in case if students have not completely and correctly filled the data tables.**

**Note that these marks are max in each category. We may assign less than the given percentage of marks in case students have not successfully completed all the requirements.**

**This lab is time constrained. Please note that you must finish your work and submitted duly filled handout to the lab engineer within given time.**

## LAB 06

### IMPLEMENTATION OF HALF ADDER & FULL ADDER

**Name:**

**Roll Number:**

**Date:**

#### 1. Objectives:


Having completed this experiment you will be able to

- Understand the use of logic gates in arithmetic operations.
- Understand the addition of two binary digits using Logic circuit as a half adder.
- Understand the performance of combinational circuit that performs the addition of three bits (two significant bits and a previous carry) called a full-adder.

#### 2. Basic Information:

 
##### 2.1. Half Adder:

Half Adder is combinational logic circuit that generates the sum of two binary numbers (each having 1 bit length). The logic circuit has two inputs and two outputs i.e. Sum & Carry.


 
##### 2.2. Full Adder:

Full Adder is combination logic circuit that performs the sum of 3 input binary numbers, (each having 1 bit length). Two of the binary input variables are x and y represent the two significant bits to be added the third input z, represents the carry from previous lower significant position. Outputs of Full Adder are Sum and Carry represented as  $S_{FA}$  and  $C_{FA}$  respectively.



### 3. Experimental Work

#### 3.1. Material Used:

- Connecting wires
- Logic Trainer
- Components: 7432 (OR), 7408 (AND), 7486 (XOR)

#### 3.2. Procedure:

- Wire the circuit according to the pins supply indicator i.e. +5v to pin number 7, 14 respectively.
- Interconnect the basic logic gates as per logic diagrams given for half adder and full-adder
- Implement the given Boolean expression by basic logic gates, verify and write the result in the truth table

#### 3.3. Experimental Results




**Truth Table**

Inputs		Output	
X	Y	$S_{HA} = x'y + xy'$	$C_{HA} = x y$
0	0		
0	1		
1	0		
1	1		

**Truth Table**

i/p's			o/p's			
x	Y	z	S <sub>FA</sub>		C <sub>FA</sub>	
			Actual	Observed	Actual	Observed
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

3.4. Obtain the expressions for Half adder and Full adder (both sum & carry).

   **4. Pin Configuration**

**5. In Case of Trouble:**

- Check the power supply.
- Check the Vcc and GND at pin number 14 and 7 of the IC under test.
- Check all the wire connections and remove the breaks.
- Check the IC under test using truth table.