



For the above circuit:

1. Write any 3 properties of this circuit
2. Obtain state equations for the flip flops
3. Tabulate the state stable for this circuit
4. Draw state diagram

