

Fall 202 COMP 206

Assignment No.3

Due: Monday 23rd November

1. Simplify the boolean expression to minimum number of literals using Boolean algebra & draw circuits to implement both original & simplified version:

a. $xyz + x'y + xyz'$

b. $(BC' + A'D)(AB' + CD')$

2. Reduce the expression to 1 literal: $A'B(D + C'D) + B(A + A'CD)$

3. Find the complement of $F = z + z'(v'w + xy)$

4. Convert the following Boolean function in SOM, POF & POM form:

$$F(a,b,c) = a'b + a'c' + abc$$

5. For the following truth table

<i>a</i>	<i>b</i>	<i>c</i>	<i>f</i> ₁	<i>f</i> ₂
0	0	0	1	1
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	1	1	0

- a. Obtain expression for f_1 in Sum of Minterms form.
- b. Obtain expression for f_2 in product of Maxterms form & simplify using Boolean algebra