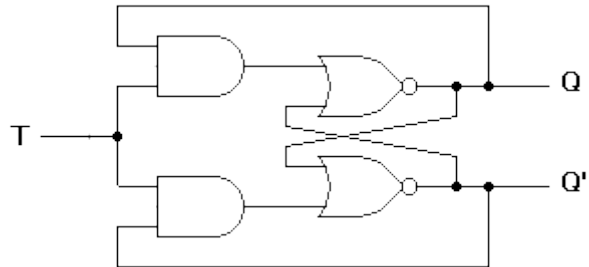



## Assignment 5 – Sequential Logic

1. Determine the characteristic table and equation for the following circuits. What is the difference in the working of both the circuits

a.



b.

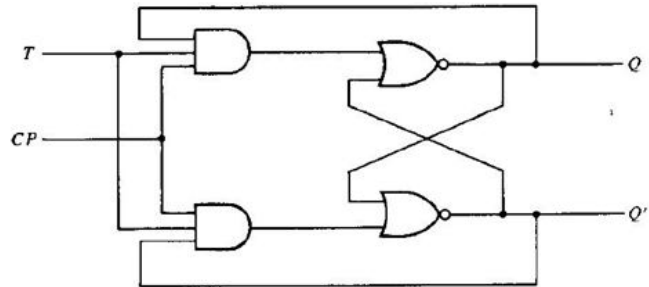

2. Determine the characteristic table for the following circuit:

